

Subject: ELECTRICAL AND ELECTRONICS, ENGG  
(MECH & CIVIL)

UNIT - I  
ELECTRICAL CIRCUITS

\* Basic deff: in ckt's :

\* Voltage :

\* According to the structure of an atom, there are two types of charges they are positive & negative charges.

\* there exists a force of attraction b/w these positive & negative charges.

\* All the opposite charges possess certain amount of potential energy because of the separation b/w them.

\* The difference in potential energy of the charges is called the potential difference.

\* potential difference in electrical terminology is known as voltage.

Deff: of Voltage :- the potential difference b/w two charges or two points is known as voltage.

\* it is denoted by " $V$ "

\* it is also defined as energy per unit charge i.e,

$$V = \frac{W}{Q}$$

where  $W$  = Energy in joules  
 $Q$  = Charge in coulombs  
 $V$  = Voltage in volts.

\* one volt is the potential difference b/w 2 points when one joule of energy is used to pass one Coulomb of charge from one point to the other.

\* Example:

if 70j of energy is available for every 30 c of charge, what is the voltage.

Sol: we know that  $V = \frac{W}{Q}$

here  $W = 70j$

$Q = 30c$


$$\therefore V = \frac{70}{30} = 2.33v.$$

\* Current:

\* There are free electrons available in all Semiconductive and Conductive Materials.

\* these free  $e^-$  move at random in all directions within the structure in the absence of external pressure or voltage.

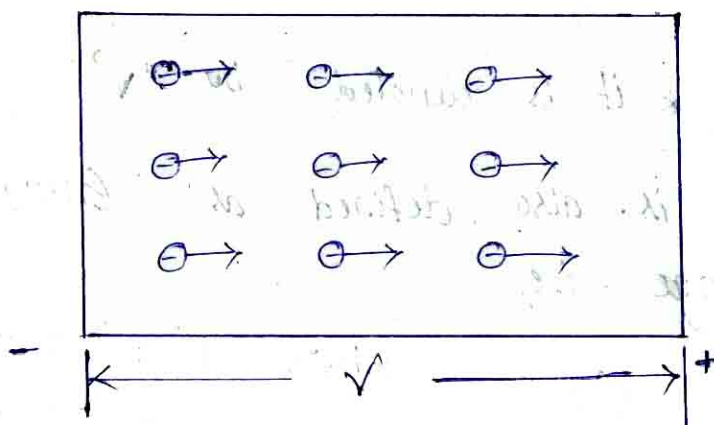\* if a certain amount of voltage is applied across the material, all the free electrons move in one direction depending on the polarity of the applied voltage shown in fig:-



- \* This Movement of  $e^-$  from one end of the Material to the other end constitutes an Electric Current.
- \* the direction of Current flow is opposite to the flow of Electrons.

Def: of Current: it is defined as the rate of flow of Electrons in a Conductive or Semiconductive Material.

- \* it is measured by the number of  $e^-$  that flow past a point in unit time.
- \* it is denoted by " $I$ "
- \* its units are Amper's ; denoted by "A"
- \* it is expressed mathematically as

$$I = Q/t$$

Where  $I$  = Current ;  $Q$  = charge of  $e^-$  ;  $t$  = time

\* Example:-

five Coulombs of charge flow past a given point in a wire in 2 Sec. How many amperes of current is flowing.

Sol: we know that  $I = Q/t$

here  $I = ?$

$$Q = 5C$$

$$t = 2sec$$

$$I = 5/2 = 2.5 A.$$



## \* power :

- \* Capacity to do work is called energy
- \*  $\therefore$  Energy is nothing but stored work.

Def: of power:- it is defined as the rate of change of energy.

- \* it is denoted by "p"

$$\text{power } (p) = \frac{\text{Energy}}{\text{time}} = \frac{W}{t} \quad (\text{or}) \quad p = \frac{dW}{dt}$$

where "dW" is change in energy.

"dt" is change in time.

$$p = \frac{dW}{dt} \Rightarrow \frac{dW}{dV} \times \frac{dV}{dt}$$

$$\Rightarrow V \times I \Rightarrow VI$$

- \* its units are watts

- \* one watt is the amount of power generated when one joule of energy is consumed in one second.

## \* Example:-

What is the power in watts if energy equal to 50 J is used in 2.5 sec?

Sol:-

we know that  $p = \frac{W}{t}$

here  $W = 50 \text{ J}$

$t = 2.5 \text{ sec}$

$$p = \frac{50}{2.5}$$

$$= 20 \text{ W}$$

## \* Classification of Network Elements :-

\* Broadly, Network Elements may be classified into four groups they are

(1) Active Elements or passive Elements

(2) unilateral or bilateral Elements.

(3) Linear (or) Non-Linear Elements

(4) Lumped (or) distributed Elements.

### (1) \* Active Elements :-

\* An Element which is Capable of Supplying power to external Elements present in the circuit for infinite time period.

\* then such Elements are called Active Elements.

#### Examples for Active Elements :-

\* Voltage Source \* Current Source.

### \* passive Elements :-

\* Elements which accept or absorb power from external devices.

\* Such Elements are called passive Elements.

#### Examples for passive Elements :-

\* Resistor

\* inductor

\* Capacitor

## ② \* Unilateral Elements:-

\* Elements having different voltage current relationship for either direction of current flow then such elements are called unilateral elements.

### Examples of Unilateral Elements:-

\* Vacuum diodes \* Silicon diodes \* Metal Rectifiers

## \* Bilateral Elements:-

Bilateral Elements are those elements whose voltage and current relationship remains unaltered for either polarity of voltage & current.

### Examples of Bilateral Elements:-


\* Resistor.

## ③ \* Linear Elements:-

\* The response of an element which obey direct proportionality with voltage or current is called linear elements.

\* An element is said to be linear element, if its voltage - current char: is at all time a straight line through the origin.

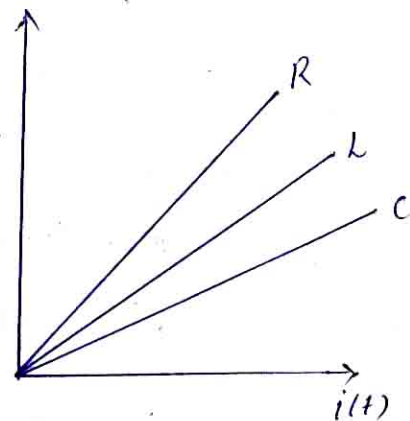\* the term linear is valid only for passive elements.



### Example for Linear Elements:-

- \* Resistor
- \* inductor
- \* Capacitor.



### \* NON linear Element :-

An element does not satisfy the direct proportionality b/w voltage & current then such elements are called non-linear elements.

### Examples for non-linear elements :-

\* diode \* transistor etc.

### (H) \* Lumped Elements :-

\* When it is possible to separate the elements of a network physically like resistor, inductor, capacitor. then such elements are called Lumped elements.

\* Kirchhoff's law are only applicable to circuit with lumped elements.

### \* Distributed Elements :-

\* When it is not possible to separate the elements of a n/w physically the elements are known as distributed elements.

### Examples for distributed elements are :-

\* Transmission line.

### \* Resistance :-

\* When a current flows in a material, the free  $e^-$  move through the material & collide with other atoms.

\* These collisions cause the  $e^-$  to lose some of their energy.

\* This loss of energy per unit charge is the drop in potential across the material.

- \* This collisions restrict the movement of the electrons.

Def:- of Resistance:- The property of a material to restrict the flow of electrons is called Resistance.

- \* it is denoted by "R"
- \* the symbol of resistor is shown in the figure.



- \* the units of resistance is "ohm"  $\Rightarrow \Omega$
- \* one ohm is the resistance offered by the material when a current of one ampere flows between two terminals with one volt applied across it.
- \* According to ohm's law voltage across the resistor is given as

$$V = IR$$

- \* Current across resistor is

$$I = V/R$$

- \* power absorbed by the resistor is

$$P = Vi$$

$$= (iR)i = i^2R$$

$$P = i^2R$$

- \* Energy lost in a resistor in time "t" is

$$W = \int_0^t P \cdot dt$$



$$\Rightarrow W = Pt$$

$$= i^2 R t$$

$$\Rightarrow \boxed{W = \frac{V^2}{R} \cdot t}$$

Where  $V$  is in Volts  
 $R$  is in Ohms  
 $t$  is in sec  
 $W$  is in joules

\* the resistance of a conductor " $R$ " varies directly with its length & inversely with the area of cross-section of the conductor, i.e.,

$$R \propto \frac{L}{a}$$

$$\Rightarrow \boxed{R = \rho \left[ \frac{L}{a} \right]}$$

Where  $R$  is the resistance in  $\Omega$   
 $L$  is the length in  $m$   
 $a$  is the area of cross-section in  $m^2$   
 $\rho$  resistivity of material.

\* Example :

a current of 5A is passed through an aluminium wire whose cross-sectional area is  $0.01 \text{ cm}^2$ . if the resistivity of aluminium is  $2.7 \times 10^{-6} \Omega \text{ cm}$  & a voltage of 200V is applied across the coil, calculate the length of the wire.

Sol :

given data

voltage applied  $V = 200 \text{ volts}$

Current  $I = 5 \text{ Amp}$

Area of cross-section  $a = 0.01 \text{ cm}^2$

resistivity of material  $\rho = 2.7 \times 10^{-6} \Omega \text{ cm}$

We know that  $V = IR$

$$R = V/I$$

$$R = \frac{200}{5} = 40 \Omega$$

But we have  $R = \rho \cdot \frac{L}{a}$

$$\therefore L = \frac{R \times a}{\rho}$$

$$= \frac{40 \times 0.01}{2.7 \times 10^{-6}} = \frac{40}{2.7 \times 10^{-4}}$$

$$\therefore L = 14.815 \times 10^4 \text{ cm}$$


### \* Inductor :

- \* A wire of certain length, when twisted into a coil becomes a basic inductor.
- \* If current is made to pass through an inductor, an electromagnetic field is formed.
- \* A change in the magnitude of the current changes the electromagnetic field.
- \* Increase in current expands the fields, & decrease in current reduces the field.
- \* which induces a voltage across the coil according to Faraday's law of electromagnetic induction.
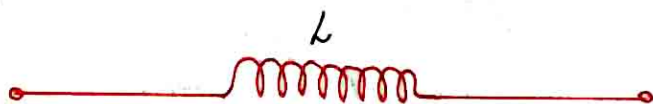
### Def: of inductance :

The property of the coil which opposes the sudden change in current through it.

\* It is the symbol of inductance is shown in the fig:



- \* it is denoted by "H".
- \* its units are henry
- \* the inductance is one henry when current through the coil, changing at the rate of one ampere per second, induces one volt across the coil.
- \* The current - voltage relation in an inductor is given by

$$V = L \frac{di}{dt}$$

where  $v$  is voltage across inductor  
 $i$  is current through "

we write the above equation as

$$di = \frac{1}{L} v dt$$

Integrating both sides, we get

$$\int_0^t di = \frac{1}{L} \int_0^t v dt$$

$$i(t) - i(0) = \frac{1}{L} \int_0^t v dt$$

$$i(t) = \frac{1}{L} \int_0^t v dt + i(0)$$

$$\Rightarrow i(t) = \frac{1}{L} \int_0^t v dt + i(0)$$

- \* from the above equation we note that the current in an inductor is dependent upon the integral of the voltage across its terminals & initial current in the coil.



\* power absorbed by inductor

$$p = vi$$

$$p = Li \frac{di}{dt} \text{ watts}$$

\* Energy stored by the inductor

$$w = \int_0^t p \cdot dt$$

$$w = \int_0^t Li \frac{di}{dt} \cdot dt$$

$$w = \frac{1}{2} Li^2$$

\* the induced voltage across an inductor is zero if the current through it is constant.

\* an inductor acts as short circuit to "DC".

\* the inductor can store finite amount of energy, even if the voltage across the inductor is zero.

\* A pure inductor never dissipates energy, so they are called non-dissipative passive elements.

\* physical inductors dissipates power due to internal resistance.

\* Example: the current in a 2H inductor varies at a rate of 2 Amp/sec. Find the voltage across the inductor & energy stored in magnetic field after 2 sec.

Sol:  $L = 2H ; \frac{di}{dt} = 4 ;$

$$V = L \frac{di}{dt} = 2 \times 4 = 8V$$

$$w = \frac{1}{2} Li^2 = \frac{1}{2} \times 2 \times (4)^2 = 16J$$


## \* Capacitance :

- \* Any two conducting surfaces separated by an insulating medium exhibit the property of a capacitor.
- \* the conducting plates are called electrodes.
- \* insulating medium is called dielectric.
- \* a capacitor stores energy in the form of an electric field or electrostatic field that is established by the opposite charges on the two electrodes.
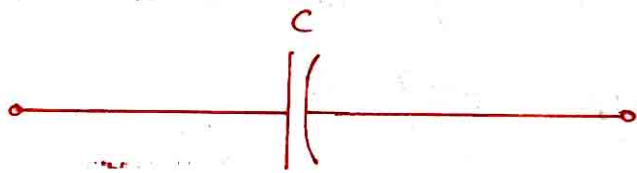
### Def: of Capacitance :

the amount of charge per unit voltage that a capacitor can store is its capacitance.

- \* the symbol of capacitance is shown in the fig:



- \* it is denoted by "C"
- \* its units are farad  $\Rightarrow$  "F"
- \* one farad is the amount of capacitance when one coulomb of charge is stored with one volt across the plates.
- \* a capacitor is said to have greater capacitance if it can store more energy or charge per unit voltage & the capacitance is given by

$$C = Q/V$$

where the above Eqn: in terms of current

$$i = C \cdot \frac{dv}{dt}$$

where  $v$  is voltage across it  
 $i$  " current through it

$$dv = \frac{1}{C} i dt$$

integrating on both sides

$$\int_0^t dv = \frac{1}{C} \int_0^t i dt$$

$$v(t) - v(0) = \frac{1}{C} \int_0^t i dt$$

$$v(t) = \frac{1}{C} \int_0^t i dt + v(0)$$

$$v(t) = \frac{1}{C} \int_0^t i dt + v(0)$$

\* the voltage in a capacitor is depends on the integral of the current through it & initial voltage across it.

\* power absorbed by the capacitor

$$p = vi$$

$$p = v c \frac{dv}{dt}$$

\* Energy stored by the capacitor

$$w = \int_0^t p dt$$

$$= \int_0^t v c \frac{dv}{dt} dt$$

$$w = \frac{1}{2} C v^2$$



- \* Current through the capacitor is zero if the voltage across it is constant.
- \* Capacitor acts as open ckt for "DC".

Example: A capacitor having a capacitance  $2\mu\text{F}$  is charged to a voltage of  $1000\text{V}$ . Calculate the stored energy in joules.

Sol:  $W = \frac{1}{2} CV^2$   
 $= \frac{1}{2} \times 2 \times 10^{-6} \times (1000)^2$   
 $= 1 \text{ joule.}$

### \* Ohm's Law:

Defn: Statement: At constant temperature the current passing through a conductor is directly proportional to the potential difference between the end of conductor (or) voltage applied across it.

from the above statement


$$I \propto V \quad (\text{or}) \quad V \propto I$$

$$V = IR$$

where "R" is proportionality constant

- \* This law in a DC ckt first discovered by German Scientist "George Simon Ohm."
- \* if the voltage is doubled then current is also doubled. So the ratio of " $V/I$ " is constant
- \* where "R" is the resistance of the conductor.

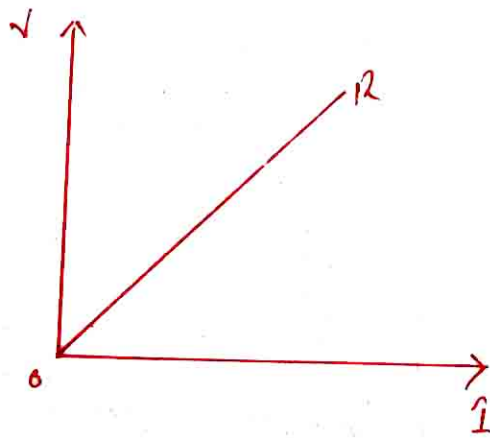\* if we draw a graph b/w  $V$  &  $I$  it will be a straight line passing through origin. Shown in the fig.



\* Ohm's law can be applied for both A.C & D.C ckt if and only if the ckt contain linear elements.

\* in case of A.C ckt, Resistance is replaced by impedance.

\* Resistance of conductor depends on:-

- \* Length of the conductor.
- \* area of cross section of conductor
- \* Resistivity of the material
- \* temperature of the conductor

\* Limitations of Ohm's law:-

\* Ohm's law can't be applied under following conditions.


- 1) when temperature of material varies
- 2) for non-linear elements
- 3) semi conductor devices.
- 4) vacuum tubes & gas filled valves.
- 5) for fluorescent lamps.

## \* Kirchhoff's Voltage Law:

Statement: Kirchhoff's Voltage Law states that the algebraic sum of all branch voltages around any closed path in a circuit is always zero at all instant of time.

\* When the current passes through a resistor, there is a loss of energy & therefore, a voltage drop.

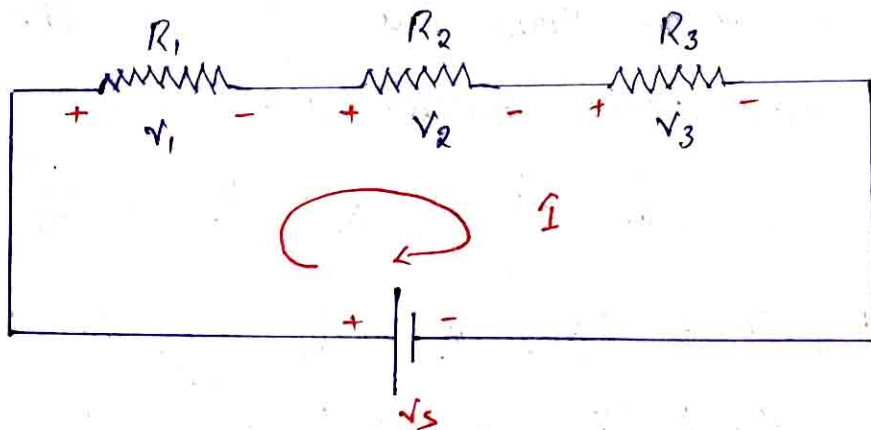
\* In any element, the current always flows from higher potential to lower potential.



- \* Consider the cut shown in the fig:-
- \* The sum of the voltage drop around the loop is equal to the total voltage in that loop.


$$V_s = V_1 + V_2 + V_3$$

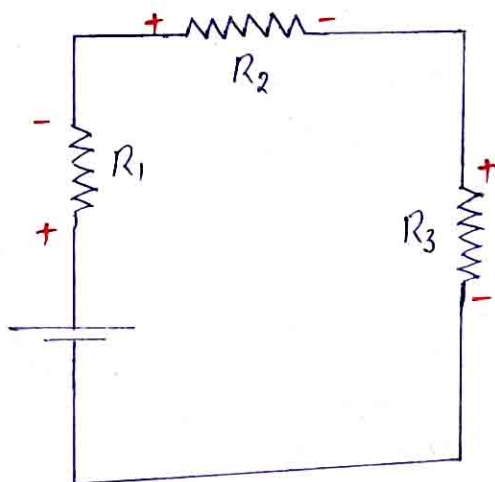\* Consider the ckt shown in the below fig. finding out the current supplied by the source "V"





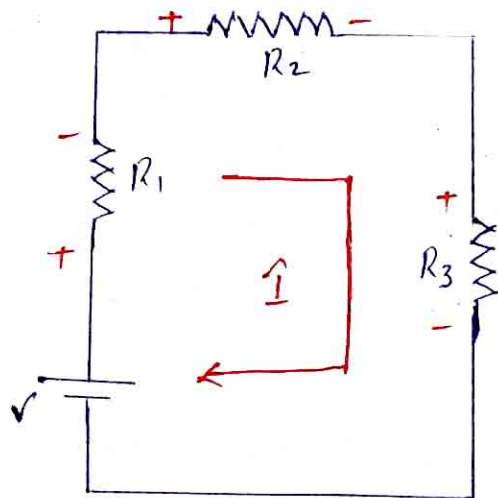- \* first step is to assume the reference current direction and to indicate the polarities for different elements. shown in the fig:-



By using Ohm's law, we find the voltages across each resistor as follows:

$$V_{R_1} = I R_1 ; V_{R_2} = I R_2 ; V_{R_3} = I R_3$$

- \* where  $V_{R_1}$ ,  $V_{R_2}$  &  $V_{R_3}$  are the voltages across  $R_1$ ,  $R_2$ ,  $R_3$  respectively.

- \* By applying KVL we can form an equation

$$V = V_{R_1} + V_{R_2} + V_{R_3}$$


$$V = I R_1 + I R_2 + I R_3$$

- \* from the above equation the current delivered from the source is

$$I = \frac{V}{R_1 + R_2 + R_3}$$

- \* Sequential Steps for KVL:-

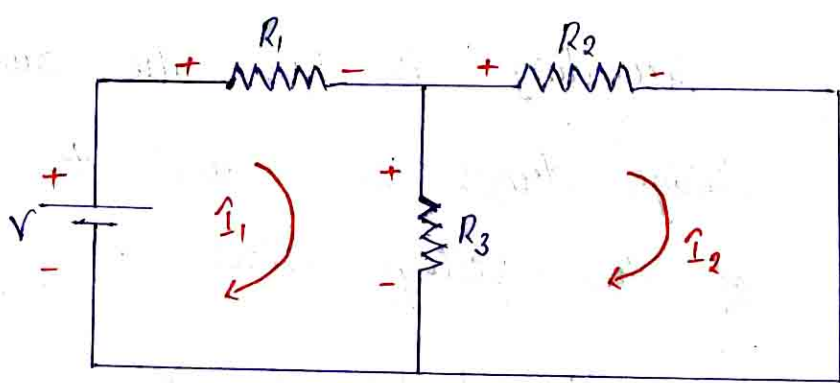- \* consider the ckt show in the fig: & write the loop equations



- \* trace the no: of closed paths in a given ckt.
- \* Assume the direction of currents in different loops.
- \* Apply KVL to every loop & write the loop equation for voltage.
- \* By loop currents we can find branch current also.
- \* if there are "n" loops then "n" equations are required for determining the loop current.
- \* the polarity of the voltage is taken as "+ve" at the point where current enters into element.


\* Applying KVL for Loop (1) in the fig:

$$V = I_1 R_1 + R_3 [I_1 - I_2]$$

\* Applying KVL for loop (2) in the fig

$$0 = I_2 R_2 + R_3 [I_2 - I_1]$$

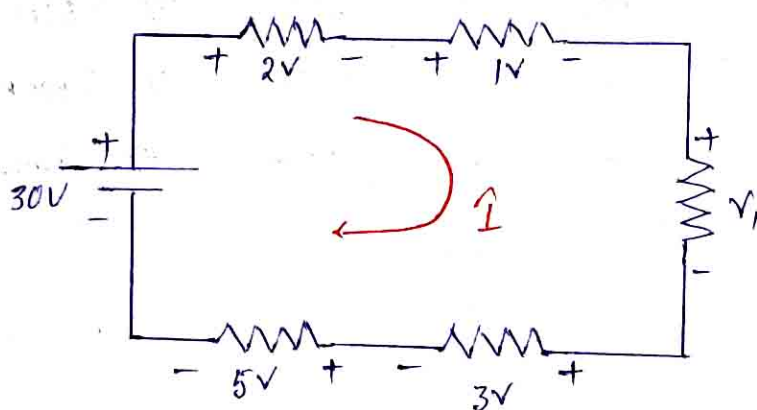\* Example: for the ckt shown in the fig: determine the unknown voltage drop "V".




Sol:

According to KVL the sum of the voltage drops is equal to the sum of the voltage rises.

$$30 = 2 + 1 + V_1 + 3 + 5$$

$$V_1 = 30 - 11 = 19 \text{ volts}$$

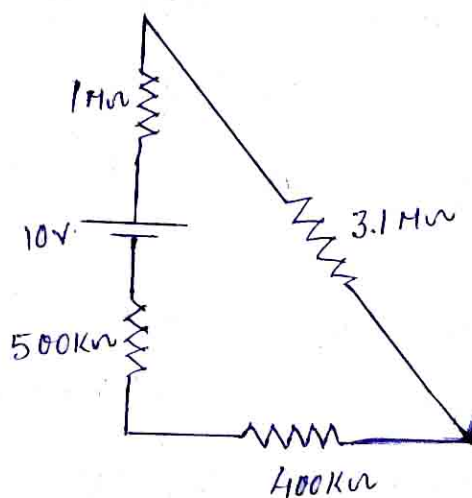\* Example: what is the current in the ckt shown in the fig. determine the voltage across each resistor.



Sol:

we assume current " $I$ " in the clockwise direction & indicate polarities as shown in below fig:

\* By using Ohm's law, we find the voltage drops across each resistor.


Voltage drop across

$$1 \text{ M resistor} = I$$

$$\text{Voltage drop across } 3.1 \text{ M}\Omega \Rightarrow \sqrt{3.1 \text{ M}} = 3.1 I$$

$$\text{" " " } 500 \text{ k}\Omega \Rightarrow \sqrt{500 \text{ k}} = 0.5 I$$
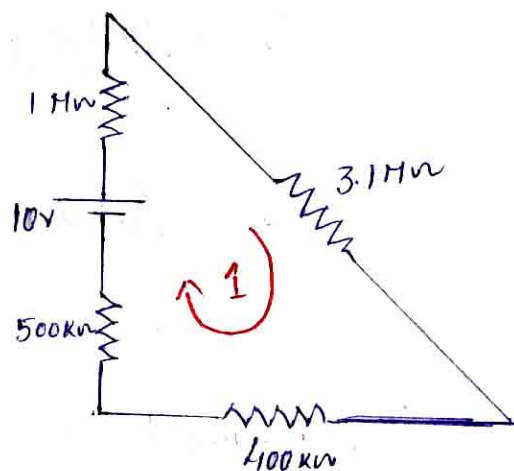
$$\text{" " " } 400 \text{ k}\Omega \Rightarrow \sqrt{400 \text{ k}} = 0.4 I$$





Now by Applying the KVL we form Eqn:-

$$10 = \hat{i} + 3.1\hat{i} + 0.5\hat{i} + 0.4\hat{i}$$

$$5\hat{i} = 10$$

$$\hat{i} = 2 \mu\text{Amp.}$$

$\therefore$  Voltage across Each Resistor is

$$V_{1M} = 1 \times 2 = 2 \text{ V}$$


$$V_{3.1} = 3.1 \times 2 = 6.2 \text{ V}$$

$$V_{400k} = 0.4 \times 2 = 0.8 \text{ V}$$


$$V_{500k} = 0.5 \times 2 = 1 \text{ V}$$

\* Example: From the ckt shown below find

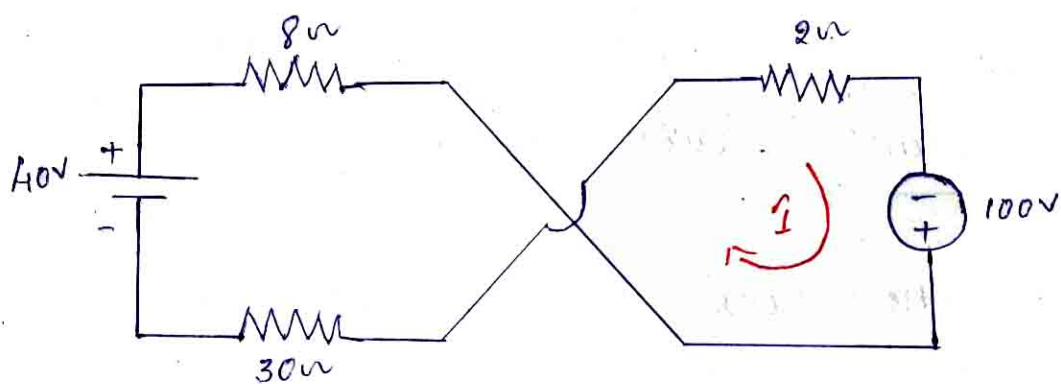(a) the current  $\hat{i}$  (b) Voltage across  $30\Omega$ .



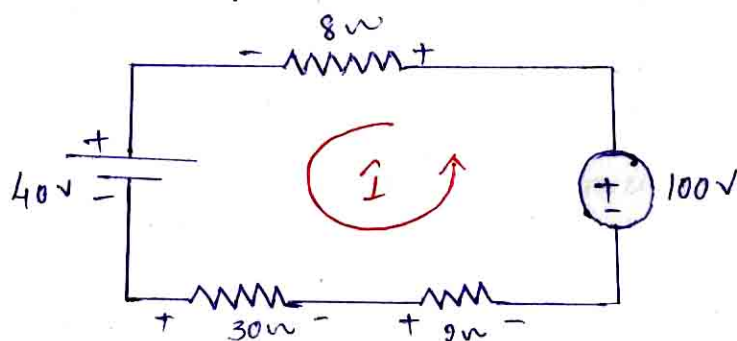Sol: we redraw the ckt as shown in the below fig: by assume current direction & indicate the polarities of resistors.



By using Ohm's law the voltage across Each resistor

$$V_8 = 8\hat{i}$$

$$V_{30} = 30\hat{i}$$

$$V_2 = 2\hat{i}$$

By applying Kirchhoff's law

$$100 = 8i + 40 + 30i + 2i$$

$$40i = 60$$

$$i = 1.5A$$


$\therefore$  Voltage drop across  $30\Omega$

$$V_{30} = 30 \times 1.5 = 45V$$
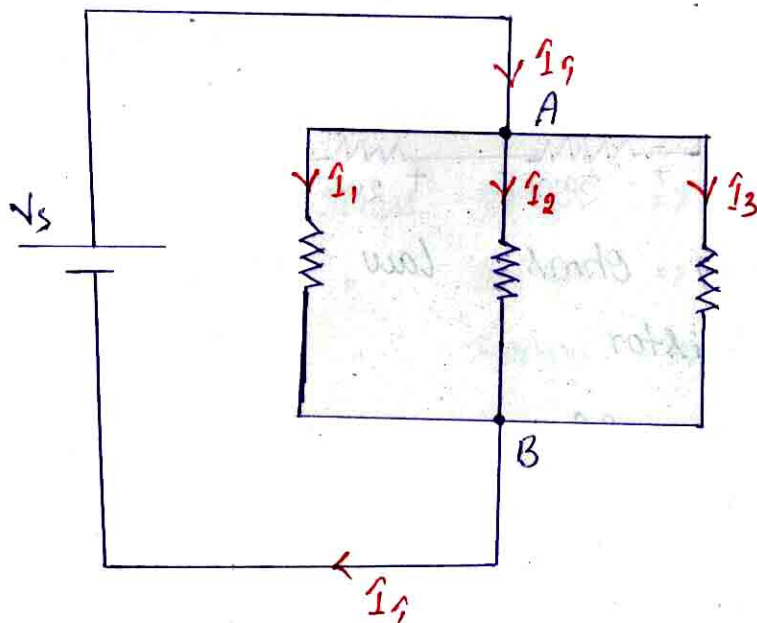
### \* Kirchhoff's Current Law:

Statement: Kirchhoff's current law states that the sum of the currents entering into any node is equal to the sum of the currents leaving that node.

- \* the node may be interconnection of two or more branches.
- \* In parallel ckt, the node is a junction point of two or more branches.
- \* total current entering into a node is equal to the current leaving that node.



\* Consider the ckt shown in the 'big' which contains two nodes "A" & "B".

\* The total current " $\hat{I}_f$ " entering node "A" is divided into  $\hat{I}_1$ ,  $\hat{I}_2$  &  $\hat{I}_3$ .

\* These currents flow out of node "A".


\* According to KCL, the current into node "A" is equal to the total current out of node "A".

$$\text{i.e., } \hat{I}_f = \hat{I}_1 + \hat{I}_2 + \hat{I}_3$$

\* If we consider node "B", all three currents  $\hat{I}_1$ ,  $\hat{I}_2$ ,  $\hat{I}_3$  are entering B, & the total current " $\hat{I}_f$ " is leaving node B.

\*  $\therefore$  KCL at Node "B" is same as node "A"
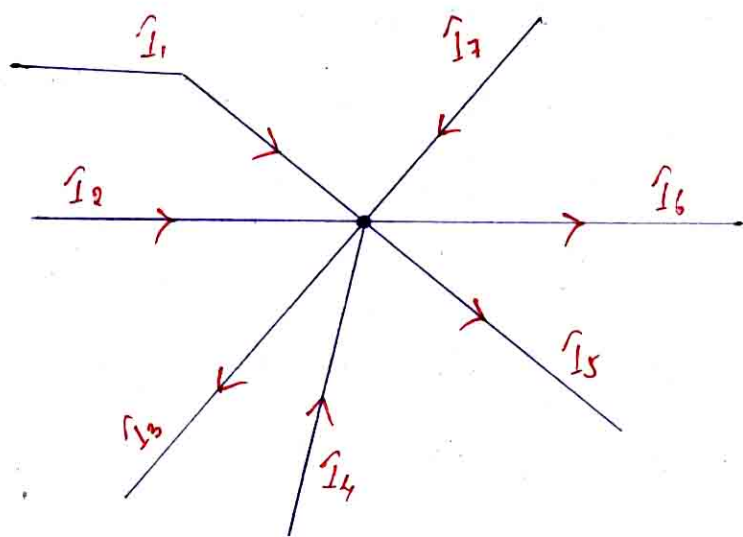
$$\hat{I}_f = \hat{I}_1 + \hat{I}_2 + \hat{I}_3$$



\* In general, Sum of the currents entering any point or node or junction equal to sum of the currents leaving from the point or node or junction. Shown in 'big':


$$\hat{I}_1 + \hat{I}_2 + \hat{I}_4 + \hat{I}_7 = \hat{I}_3 + \hat{I}_5 + \hat{I}_6$$

\* if all the terms on the right side are brought over to the left side, then the above equation can be written as

$$\hat{I}_1 + \hat{I}_2 + \hat{I}_4 + \hat{I}_7 - \hat{I}_3 - \hat{I}_5 - \hat{I}_6 = 0$$

\* this means the algebraic sum of all the currents meeting at a junction is equal to zero.

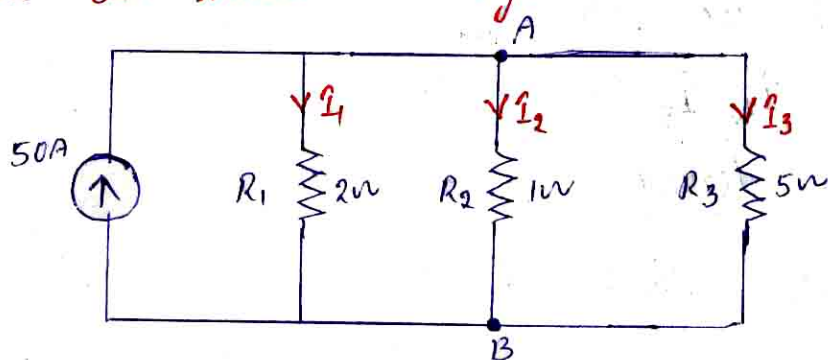\* Example: Determine the current in all resistors in the cut shown in fig:



Sol: the above cut consists of single node "A" with reference node "B".

According to Ohm's law current passing through each element:

$$\hat{I}_1 = V/2 ; \hat{I}_2 = V/1 ; \hat{I}_3 = V/5$$

By applying KCL we have

$$\hat{I} = \hat{I}_1 + \hat{I}_2 + \hat{I}_3$$

$$\hat{I} = V/2 + V/1 + V/5$$

$$50 = V \left[ \frac{1}{2} + \frac{1}{1} + \frac{1}{5} \right]$$

$$50 = V [0.5 + 1 + 0.2]$$

$$V = \frac{50}{1.7} = \frac{500}{17} = 29.41V$$

if we know the voltage at node "A" then we can find currents across each element by using K.O. Ohm's law



Current in 2Ω resistor

$$I_1 = 29.41 / 2 = 14.705 A$$

$$I_2 = V / R_2 = V / 1 = 29.41 A$$


$$I_3 = \frac{29.41}{5} = 5.882 A$$

\* Series and parallel ckt's:-

\* Series connection of Resistance:-

\* A ckt in which resistances are connected end to end is known as series ckt.

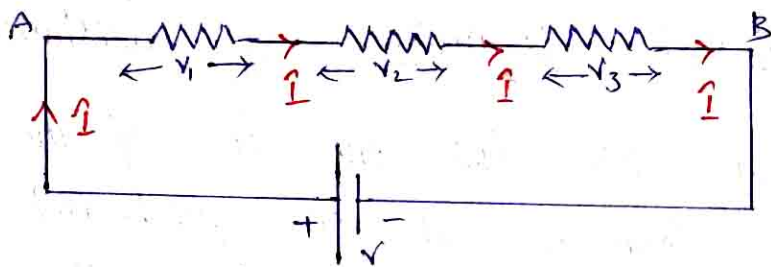\* there is only one path of current to flow in a series ckt. Shown in the fig:



Applying Ohm's law to individual resistors

$$\text{Voltage across "R}_1\text{" is } V_1 = I R_1$$

$$\text{" " " "R}_2\text{" " } V_2 = I R_2$$

$$\text{" " " "R}_3\text{" " } V_3 = I R_3$$

Total voltage  $V =$  Sum of individual voltage

$$V = V_1 + V_2 + V_3$$


$$= I R_1 + I R_2 + I R_3$$

$$V = I [R_1 + R_2 + R_3]$$

$$V / I = R_1 + R_2 + R_3$$

$$\therefore \text{Total Resistance} = R_T = R_1 + R_2 + R_3$$

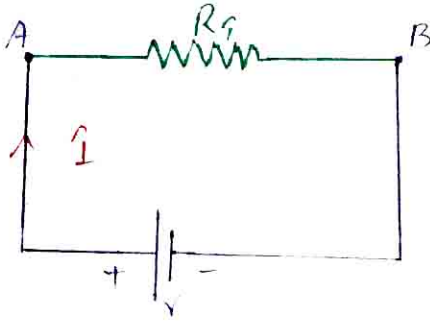\* the ckt shown in the previous page can be redrawn as shown below.




where  $R_T$  is total resistance

\* In series connection current is same through out the ckt.

\* In series connection voltage is different across each element.

\* parallel connection of resistance:-

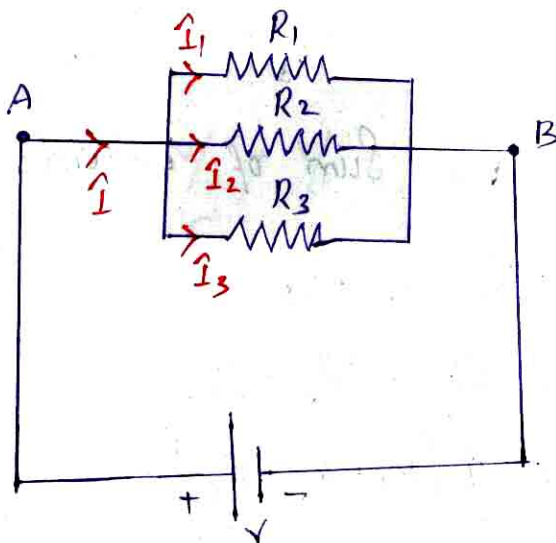\* In the ckt one end of the all the elements are connected at one point (A) & similarly the other end of all the elements are brought to another point (B) which is shown in the fig:



Applying ohm's law to individual resistors

Current flowing through resistor  $R_1$  is

$$I_1 = V/R_1$$

Current flowing through resistor  $R_2$  is

$$I_2 = V/R_2$$

Current flowing through resistor  $R_3$  is

$$I_3 = V/R_3$$

$\therefore$  Total current in the ckt is equal to sum of individual current flowing through resistors

$$I = I_1 + I_2 + I_3$$


$$= V/R_1 + V/R_2 + V/R_3$$

$$= V \left[ 1/R_1 + 1/R_2 + 1/R_3 \right]$$

$$I/V = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$

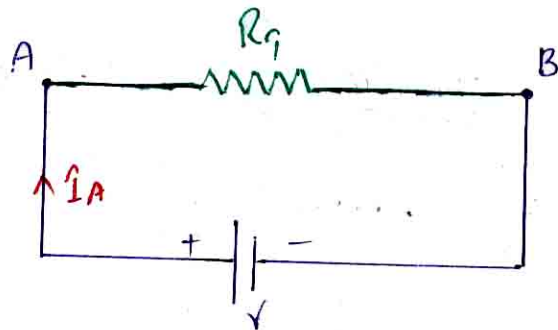$\therefore$  the ckt shown above can be redrawn as




where " $R_T$ " is equal resistance

\* in this connection voltage is same across each resistor.

\* in this connection current is different through each element.

\* Series Connection of inductance:

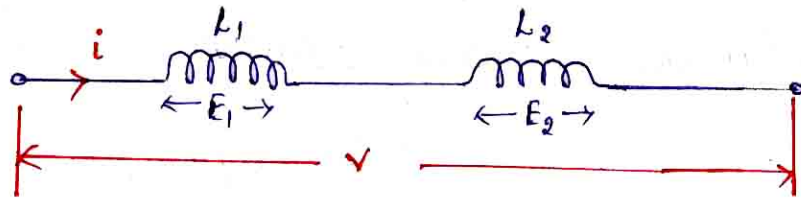

\* Consider the above fig: where two inductances are connected in series.

Let "V" be the applied voltage =  $E_1 + E_2$

Where "E<sub>1</sub>" & "E<sub>2</sub>" are EMF induced in "L<sub>1</sub>" & "L<sub>2</sub>" respectively.

∴ EMF induced is back EMF we taken as  $-[E_1 + E_2]$


$$\begin{aligned} V &= -(E_1 + E_2) \\ &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} \\ &= [L_1 + L_2] \frac{di}{dt} \\ &= L \frac{di}{dt} \end{aligned}$$

Where  $L = L_1 + L_2$

∴ inductance connected in series, its equivalent inductance is given as

$$L_T = L_1 + L_2$$

\* parallel Connection of inductance:

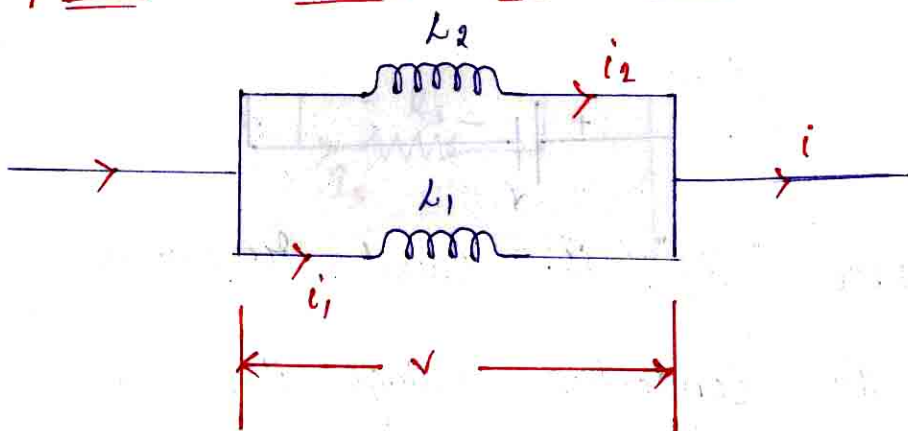


\* Consider the above fig: where two inductances are connected in parallel



Total inductance of the combination is

$$L = \frac{L_1 \times L_2}{L_1 + L_2}$$

\* Series Connection of Capacitors:

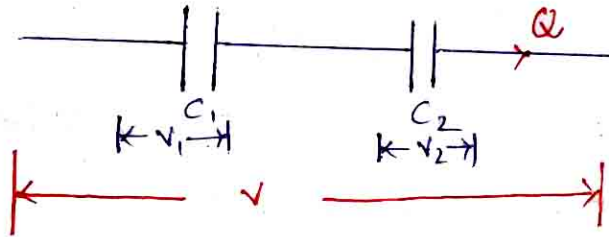

Consider two capacitors in series as shown in fig

$$V = V_1 + V_2$$

Let "Q" be the charge through each capacitor

$$Q = C_1 V_1$$

$$Q = C_2 V_2$$

Let "C" be the equivalent capacitance of the combination


$$V = \frac{Q}{C_1} + \frac{Q}{C_2} = Q \left[ \frac{C_1 + C_2}{C_1 C_2} \right] = Q C$$

where

$$C = \frac{C_1 C_2}{C_1 + C_2}$$

The above show is the equivalent capacitance of series capacitor.

\* parallel combination of capacitors:

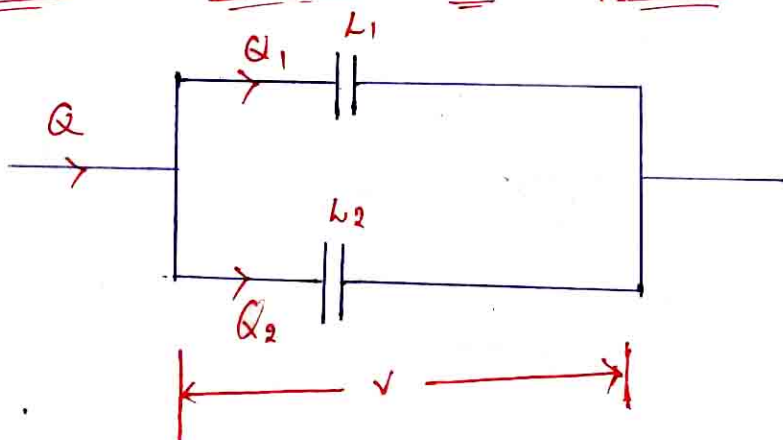

Consider the Capacitors Connected in  $\parallel$  as shown in fig.

$$\begin{aligned} Q &= Q_1 + Q_2 \\ &= C_1 V_1 + C_2 V_2 \\ &= (C_1 + C_2) V \\ &= CV \end{aligned}$$


Where  $C = C_1 + C_2$

the Equivalent Capacitance of Capacitor in  $\parallel$


$$C_{\text{equiv}} = C_1 + C_2$$
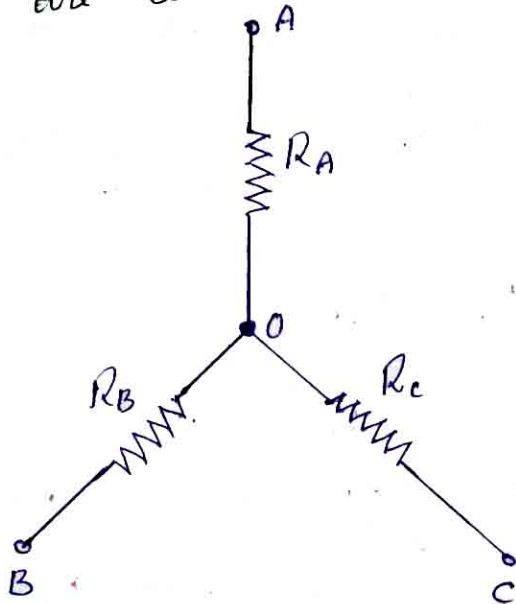
### \* Star to Delta Transformation :-

- \* Star to delta transformation is another technique useful in solving complex networks.
- \* Basically, any three ckt elements (i.e., resistor, inductor, capacitor, may be connected in two different ways.
- \* One way of connecting these elements is called the star connection or the "Y" connection.
- \* The other way of connecting these elements is called the delta ( $\Delta$ ) connection.
- \* The ckt is said to be star connection, if three elements are connected as shown in fig:



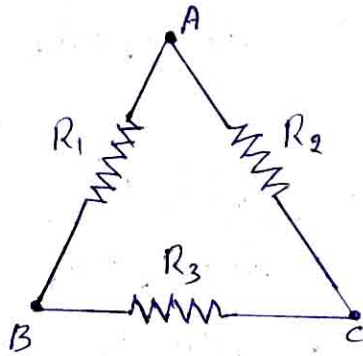\* The cut is said to be in delta connection, if three elements are connected as shown in fig.



\* The above two cut are equal if their respective resistances from the terminals AB, BC & CA are equal.

\* Consider the star connected ckt in fig:

\* The resistance from the terminals AB, BC & CA respectively are

$$R_{AB}(Y) = R_A + R_B$$

$$R_{BC}(Y) = R_B + R_C$$

$$R_{CA}(Y) = R_C + R_A$$

\* Similarly, in the delta connected n/w shown in fig: the resistances seen from the terminals AB, BC & CA respectively are

$$R_{AB}(\Delta) = R_1 \parallel (R_2 + R_3) = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$

$$R_{BC}(\Delta) = R_3 \parallel (R_1 + R_2) = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$R_{CA}(\Delta) = R_2 \parallel (R_1 + R_3) = \frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3}$$

\* Now, if we equate the resistances of star & delta ckt, we get

$$R_A + R_B = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} \longrightarrow \text{①}$$

$$R_B + R_C = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3} \longrightarrow (2)$$

$$R_C + R_A = \frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3} \longrightarrow (3)$$

\* Subtracting Eq: (2) from (1) & adding Eq: (3) to the resultant, we have

$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3} \longrightarrow (4)$$

$$R_B = \frac{R_1 R_3}{R_1 + R_2 + R_3} \longrightarrow (5)$$

$$R_C = \frac{R_2 R_3}{R_1 + R_2 + R_3} \longrightarrow (6)$$

thus, a delta connection of  $R_1, R_2$  &  $R_3$  may be replaced by a star connection of  $R_A, R_B$  &  $R_C$  from the above equations.

\* Now if we multiply the Eq: (4) & (5), (5) & (6), (6) & (4) & add the three, we get the final Eq as

$$R_A R_B + R_B R_C + R_C R_A = \frac{R_1^2 R_2 R_3 + R_3^2 R_1 R_2 + R_2^2 R_1 R_3}{(R_1 + R_2 + R_3)^2} \longrightarrow (7)$$

In Eq: (7) dividing the L.H.S by " $R_A$ " gives " $R_3$ "  
 dividing the L.H.S by " $R_B$ " gives " $R_2$ "  
 dividing the L.H.S by " $R_C$ " gives " $R_1$ "



$$R_1 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$R_2 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

$$R_3 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

\* from the above results, we can say that a star connected ckt can be transformed into a delta connected ckt & vice-versa.

\* Delta to Star transform:-

$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3}$
$R_B = \frac{R_1 R_3}{R_1 + R_2 + R_3}$
$R_C = \frac{R_2 R_3}{R_1 + R_2 + R_3}$

\* Star to delta transform:-

$R_1 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$
$R_2 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$
$R_3 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$